

De Morgan's theorem

Logic Design – section 3

Boolean algebra laws and rules:

$$A \cdot 0 = 0$$

$$A \cdot A = A$$

$$\overline{\overline{A}} = A$$

$$A \cdot 1 = A$$

$$A + A = A$$

$$A + \overline{A}B = A + B$$
$$\overline{A} + AB = \overline{A} + B$$

$$A + 0 = A$$

$$A \cdot A' = 0$$

$$A + 1 = 1$$


$$A + A' = 1$$

$$(a) \overline{B} + AB = ?$$

$$(b) B + \overline{B}C = ?$$

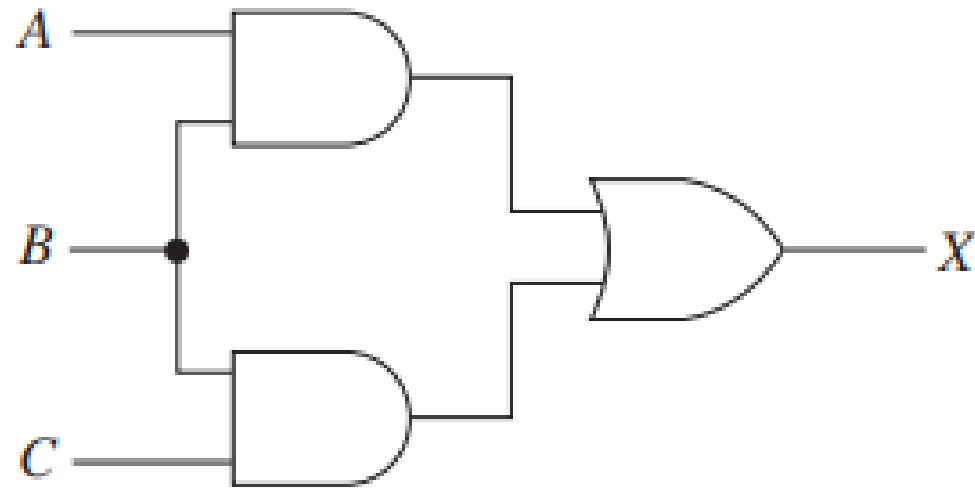Q1:


Write the Boolean equation for each of the logic circuits shown in the following figures:



Boolean equation $x = AB + BC$

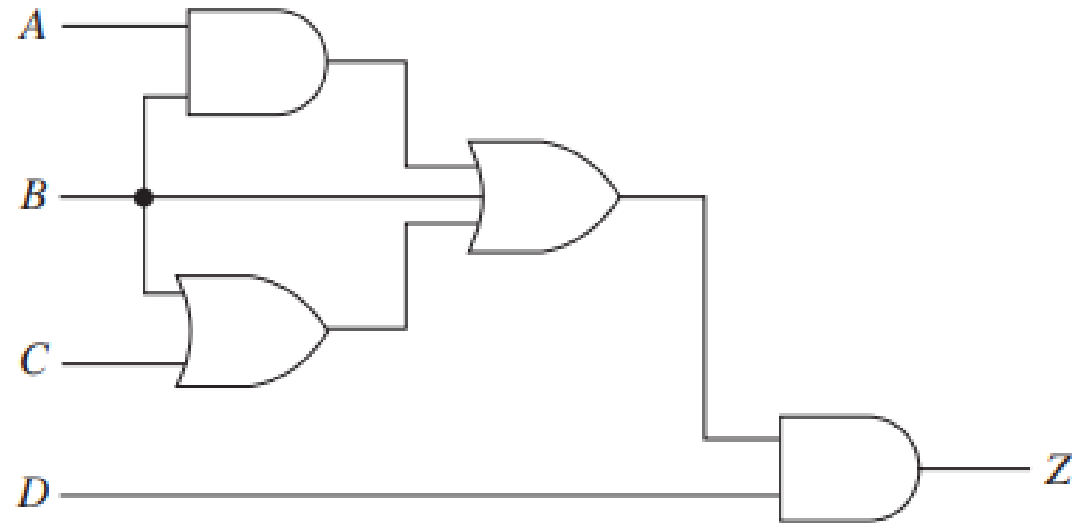Q2:


Write the Boolean equation for each of the logic circuits shown in the following figures:



Answer ??

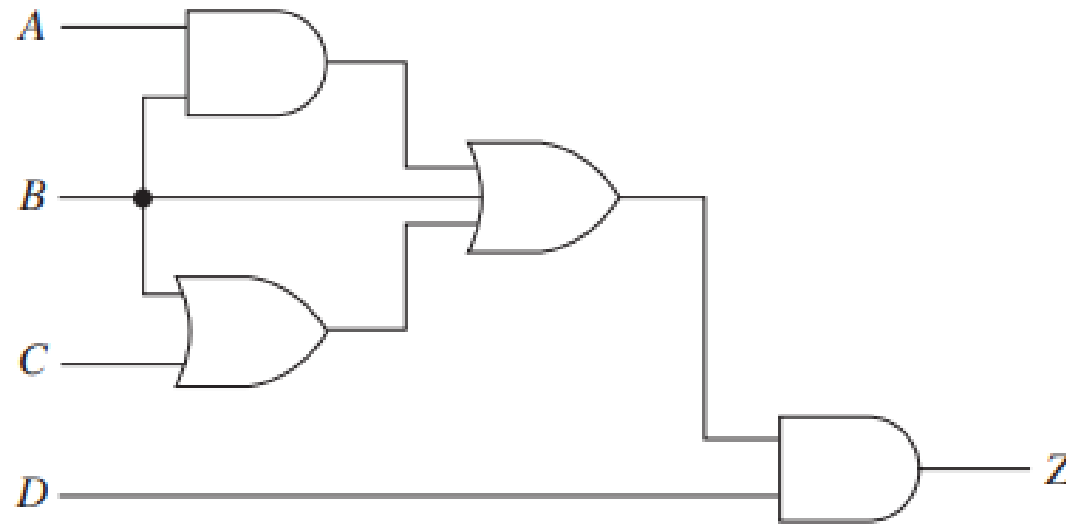Q2:

Write the Boolean equation for each of the logic circuits shown in the following figures:



Boolean equation $x = B \cdot D$

Q3:

Draw the logic circuit that would be used to implement the following Boolean equations. Also, construct a truth table for each of the equations. Simplify the equation for this problem and then draw the simplification circuit:


$$\text{a. } P = (AC + BC)(A + C)$$

Answer ??

Q3:

Answer:

a. $P = (AC + BC)(A + C)$

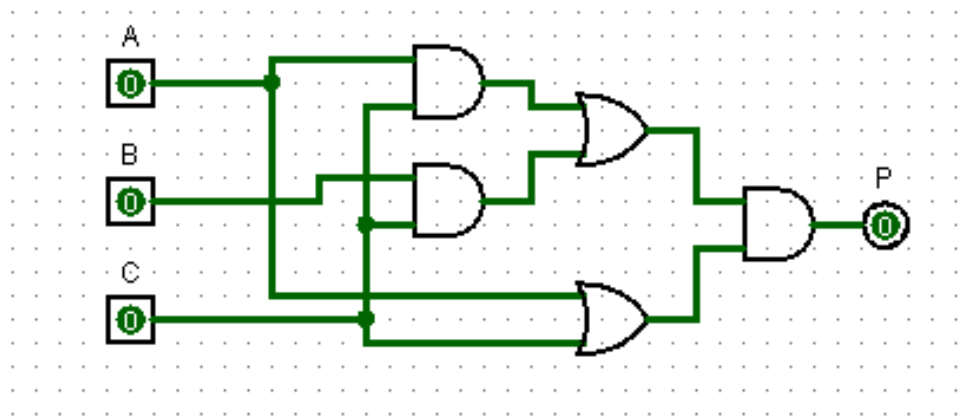


Simplified equation $x = AC + BC$

A	B	C	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

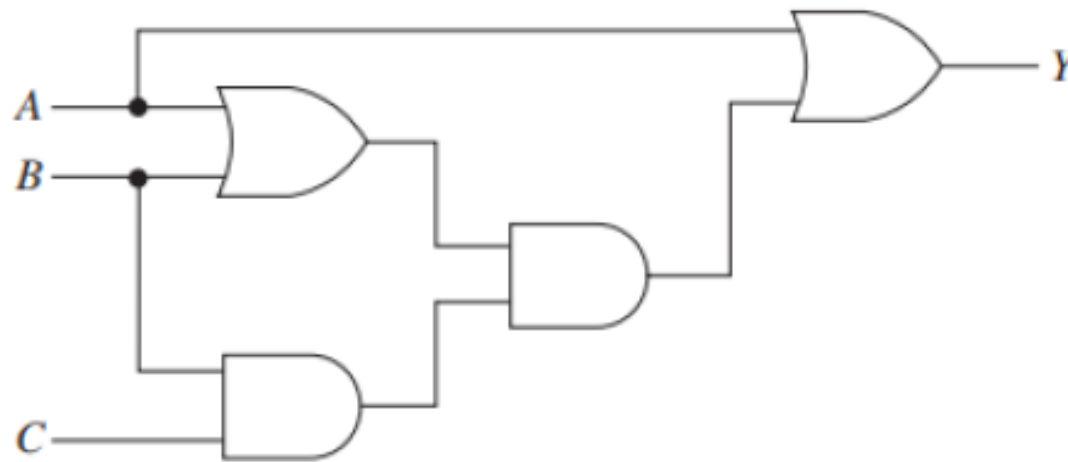Q4:


Write the equation of the circuit in the following figure, then simplify the equation, and draw the logic circuit of the simplified equation:



Simplified equation $x = ???$

Q4:

Answer:

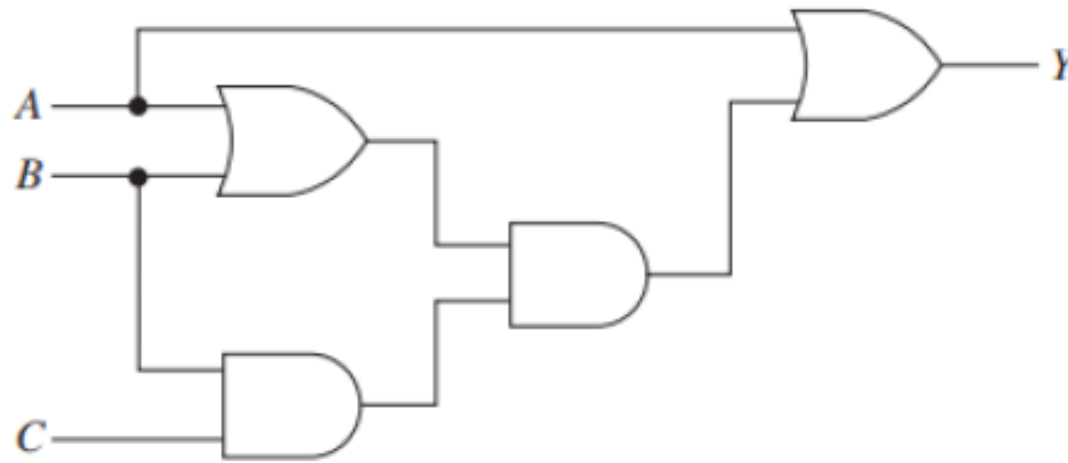

Simplified equation $x = BC + A$

The first De Morgan's theorem:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

For three variables:

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

The second De Morgan's theorem:


$$\overline{A + B} = \overline{A} . \overline{B}$$

For three variables:


$$\overline{A + B + C} = \overline{A} . \overline{B} . \overline{C}$$

Implementation of De Morgan's theorem:

De Morgan's first theorem

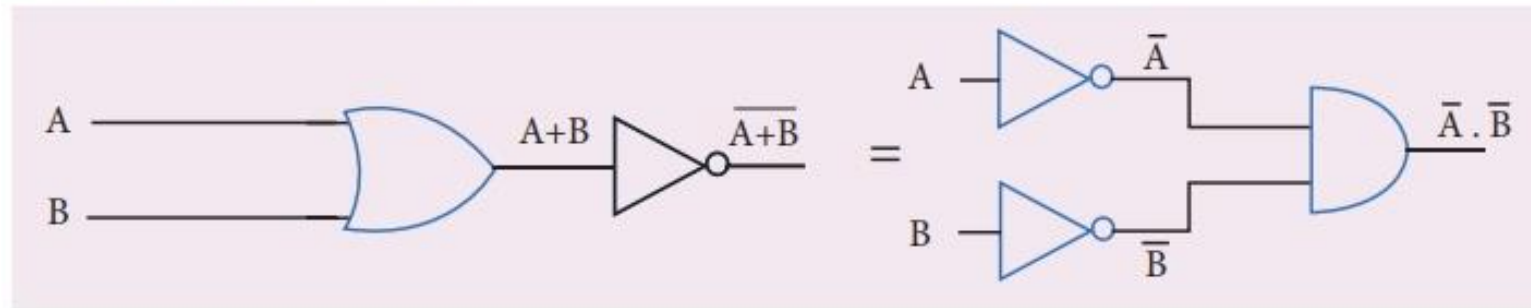


De Morgan's second theorem

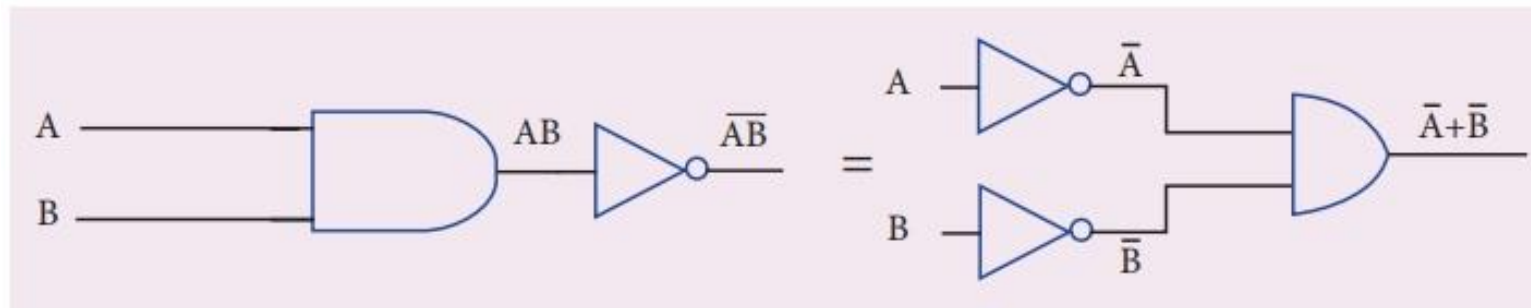

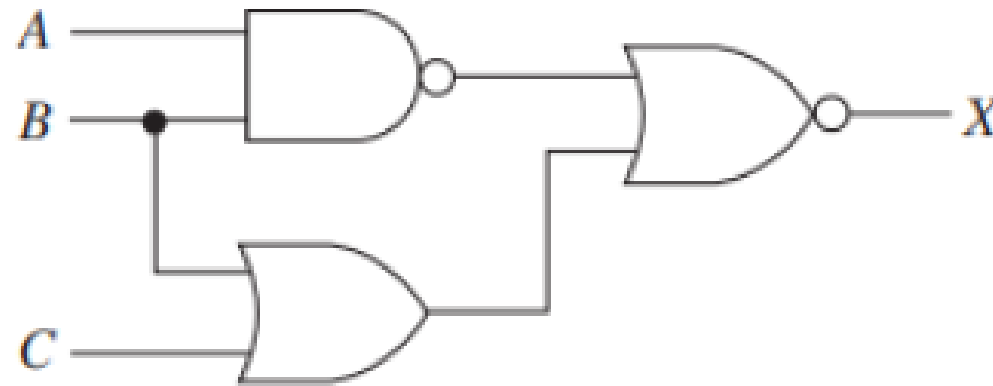Q1:


Write the Boolean equation for the circuit show in the following figure. Then, use De Morgan's theorem and then Boolean algebra rules to simplify the equation. Draw the simplified circuit



$$x = ? ?$$

Q1:

Answer:

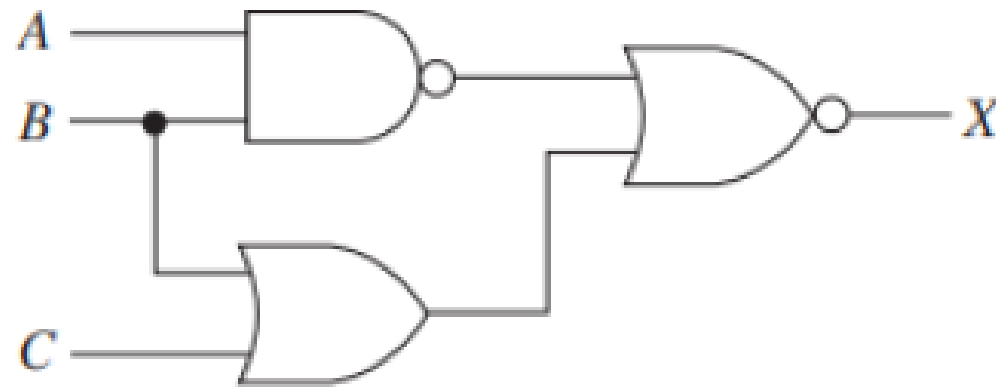


$$x = \overline{\overline{A} \overline{B}} + (B + C)$$

Simplified equation $x = 0$

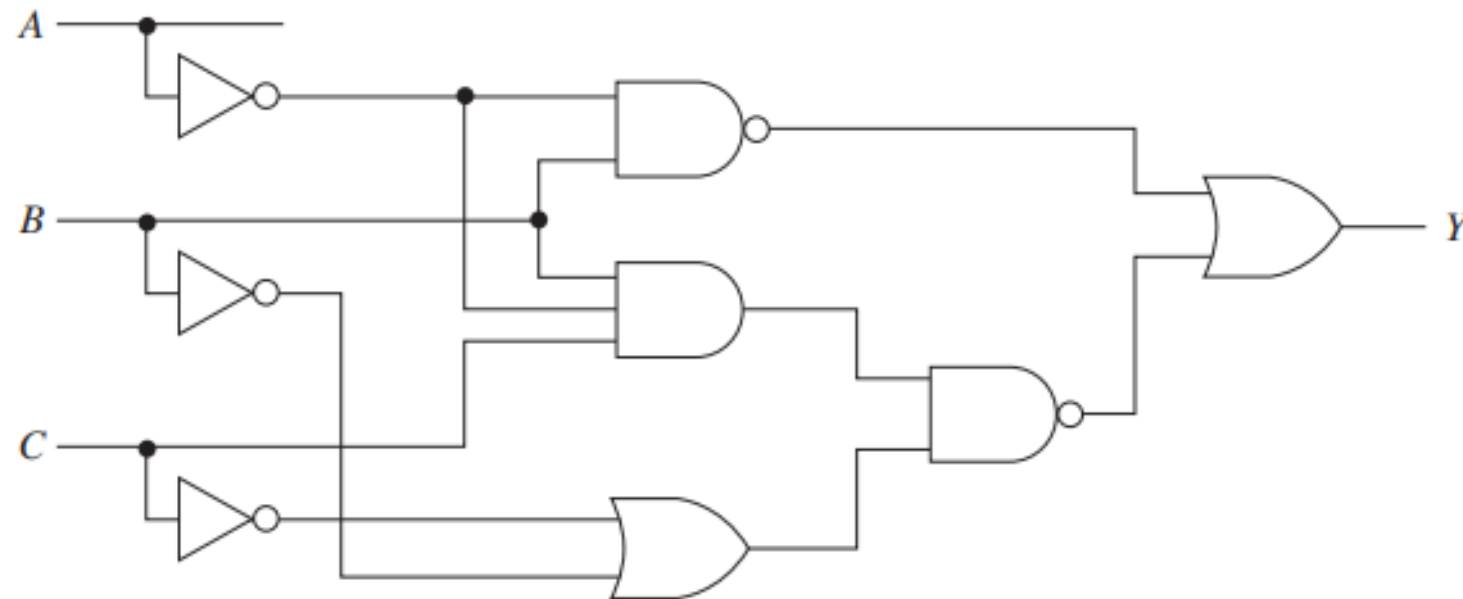Q2:


Write the Boolean equation for the circuit show in the following figure. Then, use De Morgan's theorem and then Boolean algebra rules to simplify the equation. Draw the simplified circuit



$x = ???$

Q2:


Answer:

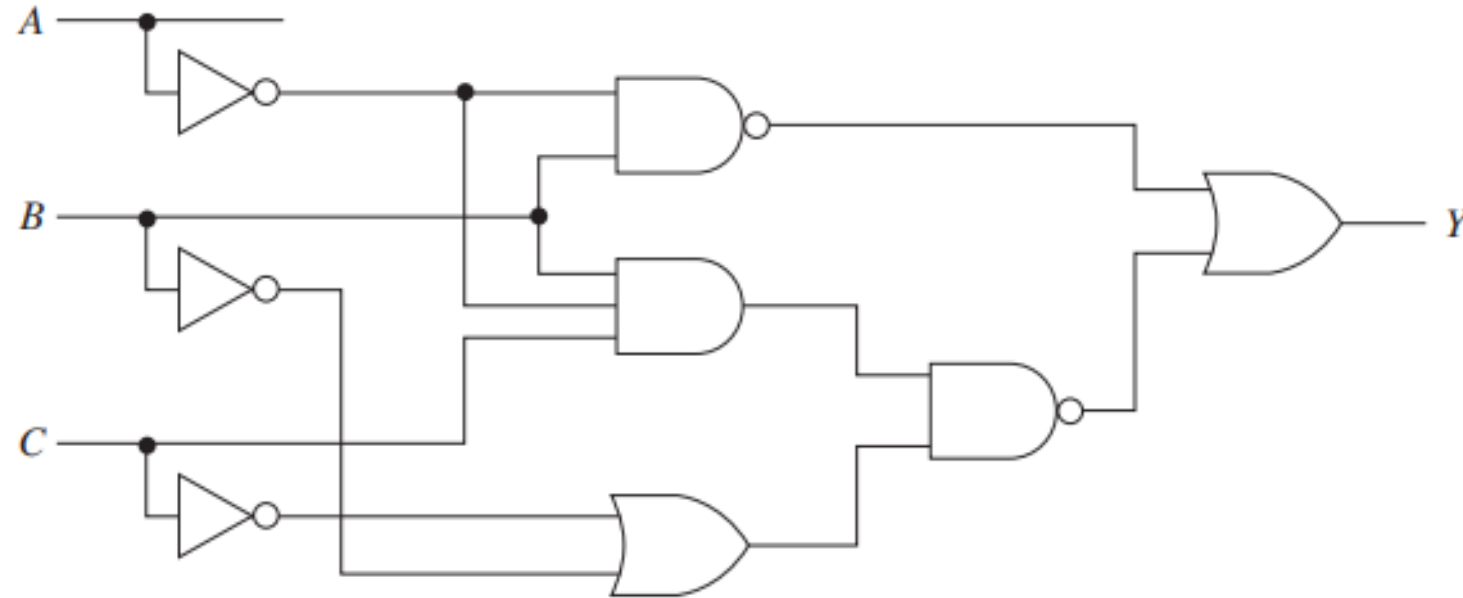

$$x = (\overline{\overline{A} B}) + \overline{\overline{A} B C. (\overline{B} + \overline{C})}$$

Simplified equation $x = 1$



Logisim

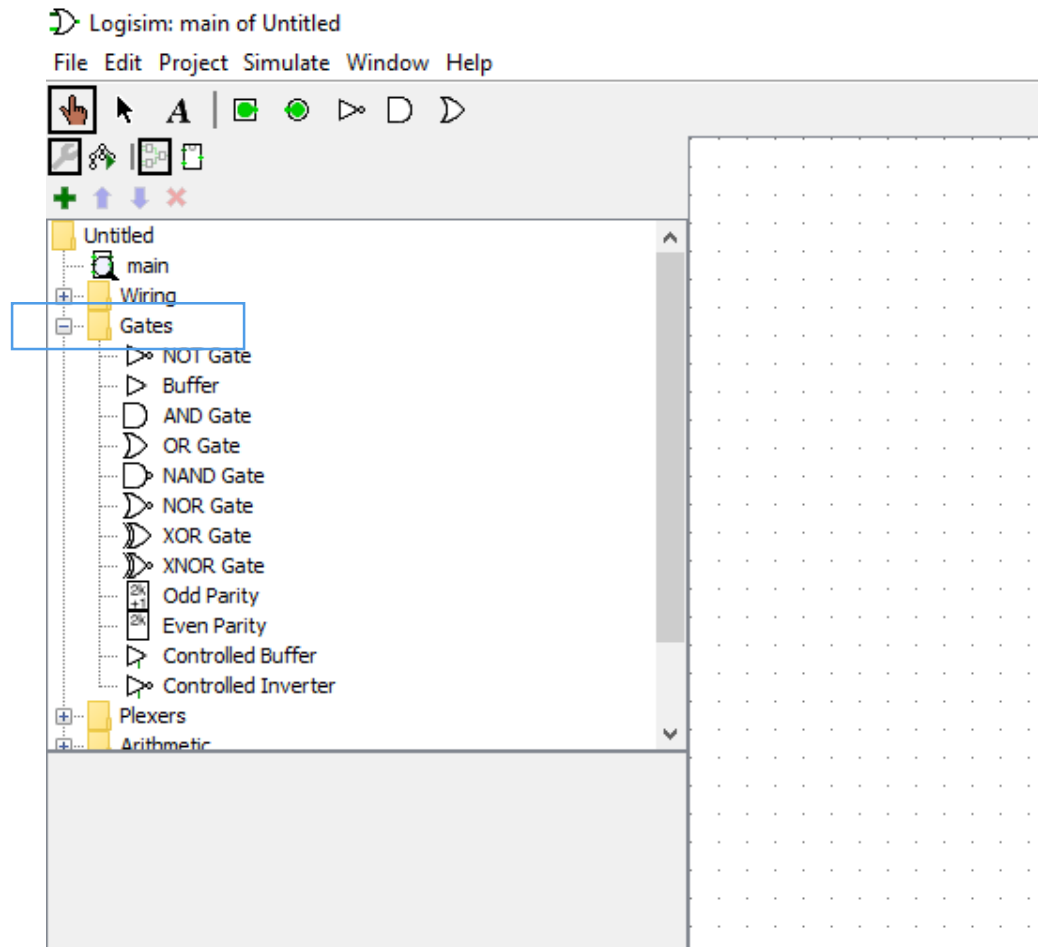

Logisim

1. NAND gate

a	b	x
0	0	1
0	1	1
1	0	1
1	1	0

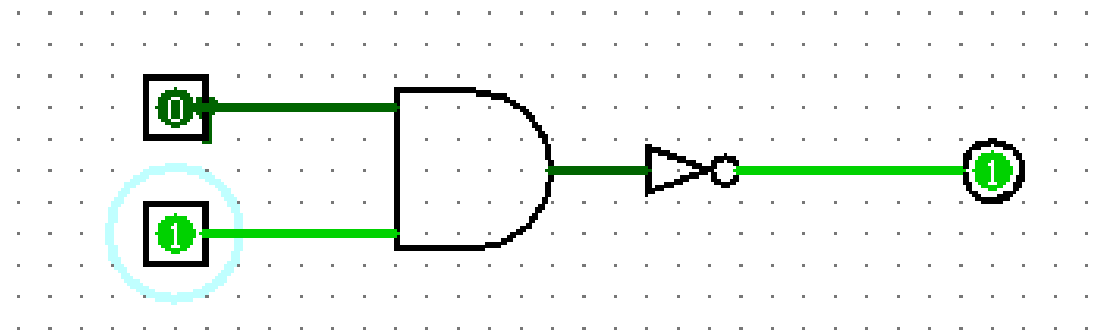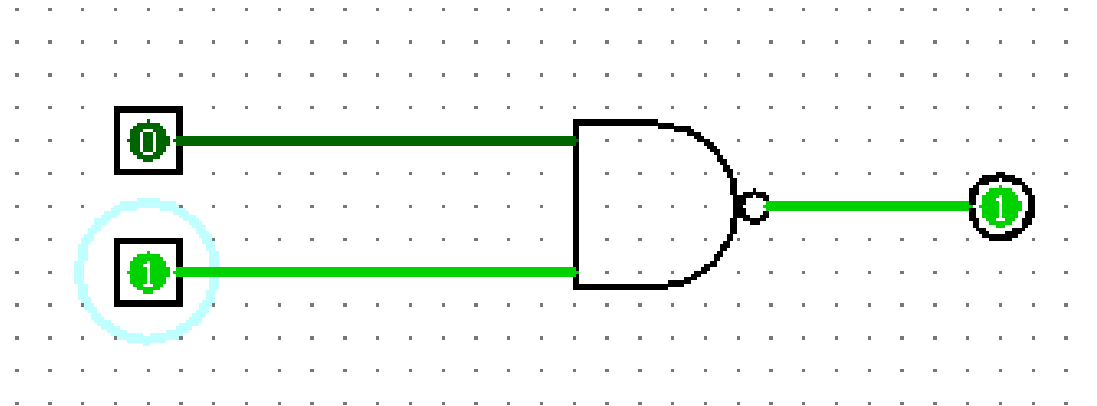

Logisim

2. NOR gate

a	b	x
0	0	1
0	1	0
1	0	0
1	1	0

